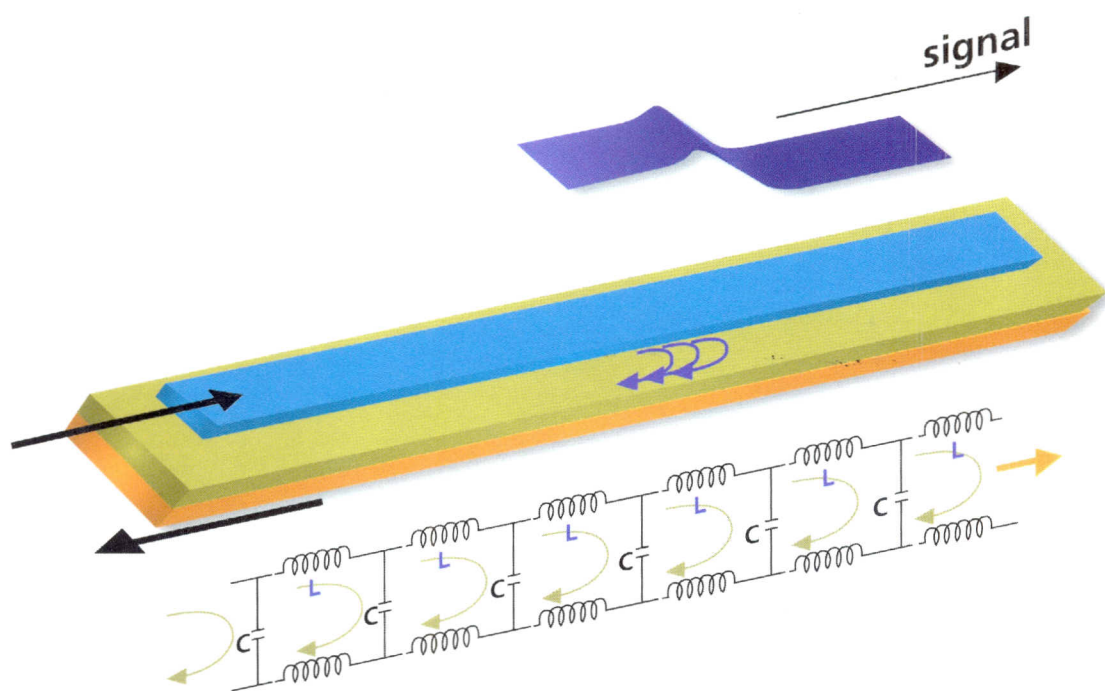


SIGNAL INTEGRITY –

Simplified



Eric Bogatin

Prentice Hall Modern Semiconductor Design Series

CONTENTS

Preface

xiii

Chapter 1

Signal Integrity Is in Your Future

1

1.1	What Is Signal Integrity?	2
1.2	Signal Quality on a Single Net	5
1.3	Cross Talk	8
1.4	Rail-Collapse Noise	10
1.5	Electromagnetic Interference (EMI)	13
1.6	Two Important Signal Integrity Generalizations	15
1.7	Trends in Electronic Products	16
1.8	The Need for a New Design Methodology	21
1.9	A New Product Design Methodology	22
1.10	Simulations	23
1.11	Modeling and Models	27
1.12	Creating Circuit Models from Calculation	29
1.13	Three Types of Measurements	34
1.14	The Role of Measurements	37
1.15	The Bottom Line	39

Chapter 2

Time and Frequency Domains

41

2.1	The Time Domain	42
2.2	Sine Waves in the Frequency Domain	44
2.3	Shorter Time to a Solution in the Frequency Domain	46
2.4	Sine Wave Features	47
2.5	The Fourier Transform	49
2.6	The Spectrum of a Repetitive Signal	51
2.7	The Spectrum of an Ideal Square Wave	53
2.8	From the Frequency Domain to the Time Domain	55
2.9	Effect of Bandwidth on Rise Time	56
2.10	Bandwidth and Rise Time	59

2.11	What Does “Significant” Mean?	61
2.12	Bandwidth of Real Signals	64
2.13	Bandwidth and Clock Frequency	66
2.14	Bandwidth of a Measurement	68
2.15	Bandwidth of a Model	70
2.16	Bandwidth of an Interconnect	71
2.17	The Bottom Line	76

Chapter 3

Impedance and Electrical Models 79

3.1	Describing Signal-Integrity Solutions in Terms of Impedance	80
3.2	What Is Impedance?	82
3.3	Real vs. Ideal Circuit Elements	84
3.4	Impedance of an Ideal Resistor in the Time Domain	86
3.5	Impedance of an Ideal Capacitor in the Time Domain	87
3.6	Impedance of an Ideal Inductor in the Time Domain	90
3.7	Impedance in the Frequency Domain	92
3.8	Equivalent Electrical Circuit Models	97
3.9	Circuit Theory and SPICE	99
3.10	Introduction to Modeling	103
3.11	The Bottom Line	108

Chapter 4

The Physical Basis of Resistance 109

4.1	Translating Physical Design into Electrical Performance	110
4.2	The Only Good Approximation for the Resistance of Interconnects	111
4.3	Bulk Resistivity	114
4.4	Resistance per Length	115
4.5	Sheet Resistance	117
4.6	The Bottom Line	121

Chapter 5

The Physical Basis of Capacitance 123

5.1	Current Flow in Capacitors	124
5.2	The Capacitance of a Sphere	126
5.3	Parallel Plate Approximation	127
5.4	Dielectric Constant	129
5.5	Power and Ground Planes and Decoupling Capacitance	130
5.6	Capacitance per Length	134
5.7	2D Field Solvers	139

5.8	Effective Dielectric Constant	142
5.9	The Bottom Line	146

Chapter 6

The Physical Basis of Inductance **147**

6.1	What Is Inductance?	147
6.2	Inductance Principle #1: There Are Circular Magnetic-Field Line Loops Around All Currents	148
6.3	Inductance Principle #2: Inductance Is the Number of Webers of Field Line Loops Around a Conductor per Amp of Current Through It	150
6.4	Self-Inductance and Mutual Inductance	152
6.5	Inductance Principle #3: When the Number of Field Line Loops Around a Conductor Changes, There Will Be a Voltage Induced Across the Ends of the Conductor	154
6.6	Partial Inductance	157
6.7	Effective, Total, or Net Inductance and Ground Bounce	163
6.8	Loop Self- and Mutual Inductance	169
6.9	The Power-Distribution System (PDS) and Loop Inductance	174
6.10	Loop Inductance per Square of Planes	179
6.11	Loop Inductance of Planes and Via Contacts	181
6.12	Loop Inductance of Planes with a Field of Clearance Holes	183
6.13	Loop Mutual Inductance	185
6.14	Equivalent Inductance	185
6.15	Summary of Inductance	187
6.16	Current Distributions and Skin Depth	189
6.17	High-Permeability Materials	198
6.18	Eddy Currents	200
6.19	The Bottom Line	202

Chapter 7

The Physical Basis of Transmission Lines **205**

7.1	Forget the Word Ground	206
7.2	The Signal	207
7.3	Uniform Transmission Lines	208
7.4	The Speed of Electrons in Copper	210
7.5	The Speed of a Signal in a Transmission Line	211
7.6	Spatial Extent of the Leading Edge	215
7.7	"Be the Signal"	216
7.8	The Instantaneous Impedance of a Transmission Line	220

7.9	Characteristic Impedance and Controlled Impedance	223
7.10	Famous Characteristic Impedances	225
7.11	<i>The Impedance of a Transmission Line</i>	228
7.12	Driving a Transmission Line	233
7.13	Return Paths	236
7.14	When Return Paths Switch Reference Planes	240
7.15	A First-Order Model of a Transmission Line	252
7.16	Calculating Characteristic Impedance with Approximations	257
7.17	Calculating the Characteristic Impedance with a 2D Field Solver	261
7.18	An n-Section Lumped Circuit Model	266
7.19	Frequency Variation of the Characteristic Impedance	273
7.20	The Bottom Line	275

Chapter 8

Transmission Lines and Reflections

277

8.1	Reflections at Impedance Changes	278
8.2	Why Are There Reflections?	280
8.3	Reflections from Resistive Loads	283
8.4	Source Impedance	286
8.5	Bounce Diagrams	288
8.6	Simulating Reflected Waveforms	289
8.7	Measuring Reflections with a TDR	292
8.8	Transmission Lines and Unintentional Discontinuities	295
8.9	When to Terminate	297
8.10	The Most Common Termination Strategy for Point-to-Point Topology	300
8.11	Reflections from Short Series Transmission Lines	302
8.12	Reflections from Short-Stub Transmission Lines	305
8.13	Reflections from Capacitive End Terminations	307
8.14	Reflections from Capacitive Loads in the Middle of a Trace	310
8.15	Capacitive Delay Adders	313
8.16	Effects of Corners and Vias	315
8.17	Loaded Lines	320
8.18	Reflections from Inductive Discontinuities	323
8.19	Compensation	328
8.20	The Bottom Line	330

Chapter 9

Lossy Lines, Rise-Time Degradation, and Material Properties

333

9.1	Why Worry About Lossy Lines	334
9.2	Losses in Transmission Lines	336

9.3	Sources of Loss: Conductor Resistance and Skin Depth	338
9.4	Sources of Loss: The Dielectric	342
9.5	Dissipation Factor	347
9.6	The Real Meaning of Dissipation Factor	350
9.7	Modeling Lossy Transmission Lines	355
9.8	Characteristic Impedance of a Lossy Transmission Line	363
9.9	Signal Velocity in a Lossy Transmission Line	365
9.10	Attenuation and the dB	367
9.11	Attenuation in Lossy Lines	372
9.12	Measured Properties of a Lossy Line in the Frequency Domain	381
9.13	The Bandwidth of an Interconnect	386
9.14	Time-Domain Behavior of Lossy Lines	392
9.15	Improving the Eye Diagram of a Transmission Line	396
9.16	Pre-emphasis and Equalization	398
9.17	The Bottom Line	399

Chapter 10

Cross Talk in Transmission Lines		401
10.1	Superposition	402
10.2	Origin of Coupling: Capacitance and Inductance	403
10.3	Cross Talk in Transmission Lines: NEXT and FEXT	405
10.4	Describing Cross Talk	407
10.5	The SPICE Capacitance Matrix	409
10.6	The Maxwell Capacitance Matrix and 2D Field Solvers	413
10.7	The Inductance Matrix	419
10.8	Cross Talk in Uniform Transmission Lines and Saturation Length	421
10.9	Capacitively Coupled Currents	426
10.10	Inductively Coupled Currents	430
10.11	Near-End Cross Talk	433
10.12	Far-End Cross Talk	436
10.13	Decreasing Far-End Cross Talk	443
10.14	Simulating Cross Talk	445
10.15	Guard Traces	452
10.16	Cross Talk and Dielectric Constant	459
10.17	Cross Talk and Timing	460
10.18	Switching Noise	464
10.19	Summary of Reducing Cross Talk	468
10.20	The Bottom Line	468

Chapter 11

Differential Pairs and Differential Impedance	471
11.1 Differential Signaling	472
11.2 A Differential Pair	476
11.3 Differential Impedance with No Coupling	478
11.4 The Impact from Coupling	482
11.5 Calculating Differential Impedance	488
11.6 The Return-Current Distribution in a Differential Pair	492
11.7 Odd and Even Modes	498
11.8 Differential Impedance and Odd-Mode Impedance	503
11.9 Common Impedance and Even-Mode Impedance	504
11.10 Differential and Common Signals and Odd- and Even-Mode Voltage Components	507
11.11 Velocity of Each Mode and Far-End Cross Talk	509
11.12 Ideal Coupled Transmission-Line Model or an Ideal Differential Pair	515
11.13 Measuring Even- and Odd-Mode Impedance	516
11.14 Terminating Differential and Common Signals	518
11.15 Conversion of Differential to Common Signals	525
11.16 EMI and Common Signals	530
11.17 Cross Talk in Differential Pairs	535
11.18 Crossing a Gap in the Return Path	537
11.19 To Tightly Couple or Not to Tightly Couple	540
11.20 Calculating Odd and Even Modes from Capacitance- and Inductance-Matrix Elements	542
11.21 The Characteristic Impedance Matrix	546
11.22 The Bottom Line	549
Appendix A	551
Appendix B	559
Appendix C	571
Index	573
About the Author	588